
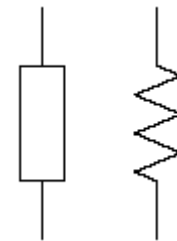


# Creative Electronics

## Resistance and Resistors
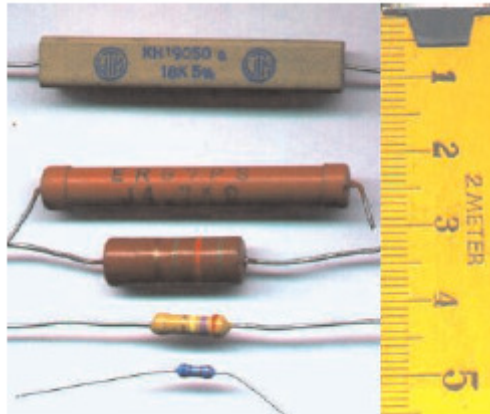
# Resistance and Resistors

- **Resistance** in electrical engineering is a measure of the degree of opposition that current is faced with.
- A **resistor** is a physical component that “implements” the definition of resistance.
- **Weerstand!**
- Conductance and conductor



Two symbols for resistors

# Relation between Voltage and Current - Ohm's Law

$$R = \frac{V}{I} \quad (3.1)$$

- **R** is the resistance of the object, measured in Ohms.
- **V** is the voltage across the object, measured in volts.
- **I** is the current through the object, measured in amperes.

# Relation between Voltage and Current

## Ohm's Law

$$R = \frac{V}{I} \quad (3.1)$$

Resistance is independent of

- the applied voltage
- the resulting current
- the frequency
- the air humidity
- the pressure

# Power Behavior

$$P = V \cdot I \quad (2.1)$$

Quantity	Unity	Symbol
Voltage, potential diff.	Volt (V)	V
Current	Ampere (A)	I
Power	Watt (W)	P

**Table 2.1:** *Electrical quantities with their respective unities and symbols.*

$$P_{resistor} = V_{resistor} \cdot I_{resistor} \quad (3.2)$$

The product of the voltage applied to a resistor and the current that flows through it results in a power  $P_{resistor}$

- $P_{resistor}$  is dissipated in the resistor.
- The dissipated power is transformed into heat.

# Power Behavior

$$P = V \cdot I \quad (2.1)$$

Ohm's law  $R = \frac{V}{I} \quad (3.1)$

$$P = \frac{V^2}{R}$$


$$P = I^2 R$$

# Using a Resistor

- **Don not overload a resistor!** Usually the low-power models can handle a power of 1/4 W or 1/3 W.
- The resistance values are **approximations!**  
They have tolerance ranges, for example  $\pm 5\%$
- **Appendix B** provides information on color codes that indicate the resistance value and tolerance.  
(what if you still cannot decide the resistance by analysing its color? — Measure it!)
- You cannot buy a resistor with arbitrary resistance value. Resistors are produced in **E-series**.  
[http://www.st-andrews.ac.uk/~jcgl/Scots\\_Guide/info/comp/passive/resistor/e12/e12.html](http://www.st-andrews.ac.uk/~jcgl/Scots_Guide/info/comp/passive/resistor/e12/e12.html)
- In order to obtain the desired resistance value, you need to combine several resistors.

# Series and Parallel Connections

## - Series Connection

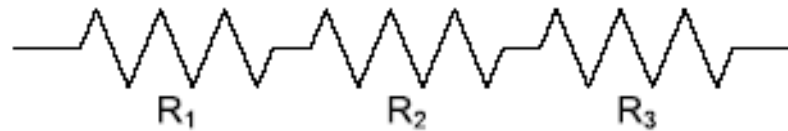

Example of a series connection

The same current flows through all the resistors.

$$R_{re} = \sum_{i=1}^N R_i. \quad (3.3)$$

$R_{re}$  is always higher than the largest (single) resistance value;

If one of the single resistance values is much higher than the other two,  $R_{re}$  is almost equal to that value;

The power dissipated in a single resistor is always lower than the power dissipated in  $R_{re}$ .




# Series and Parallel Connections

## - Series Connection

The power dissipated in a single resistor is always lower than the power dissipated in  $R_{re}$ .



$$P = I^2 R$$

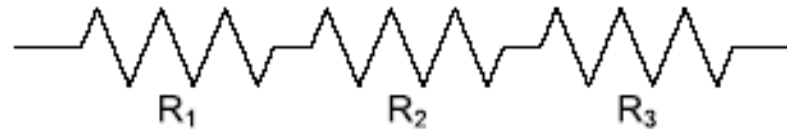


The same current flows through all the resistors.

$$R_{re} = \sum_{i=1}^N R_i. \quad (3.3)$$

$P_{re}$  – the same current on the bigger resistor  $R_{re}$ .

# Parallel Connection

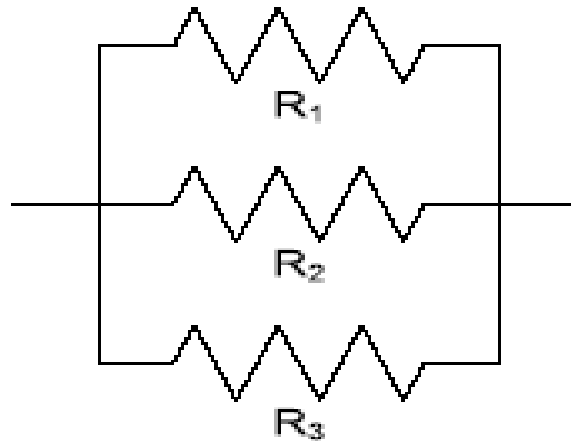

Example of a parallel connection


- The voltage over each resistor is equal.
- The current is divided over the resistors.

# Parallel Connection

$$R_{re} = \frac{1}{\sum_{i=1}^N \frac{1}{R_i}}. \quad (3.4)$$

$$\frac{1}{R_{re}} = \sum_{i=1}^N \frac{1}{R_i}$$

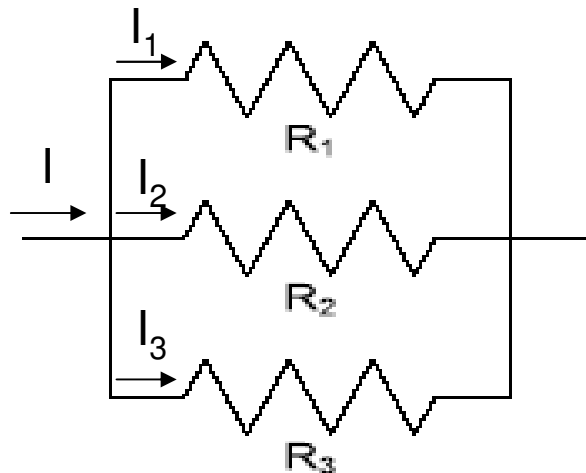- The voltage over each resistor is equal.
- The current is divided over the resistors.



$$I = \sum_{i=1}^N I_i$$

$$\frac{V}{R_{re}} = \sum_{i=1}^N \frac{V}{R_i}$$

# Parallel Connection

- The voltage over each resistor is equal.
- The current is divided over the resistors.

$$R_{re} = \frac{1}{\sum_{i=1}^N \frac{1}{R_i}}. \quad (3.4)$$

$$\frac{1}{R_{re}} = \sum_{i=1}^N \frac{1}{R_i}$$

$R_{re}$  is always lower than the lowest  $R_i$ ;

If one of the single resistance values is much lower than the other two,  $R_{re}$  is almost equal to that value;


The power dissipated in a single resistor is always lower than the power dissipated in  $R_{re}$ .

# Series and Parallel Connections - Parallel Connection

The power dissipated in a single resistor is always lower than the power dissipated in  $R_{re}$ .



$$P = \frac{V^2}{R}$$

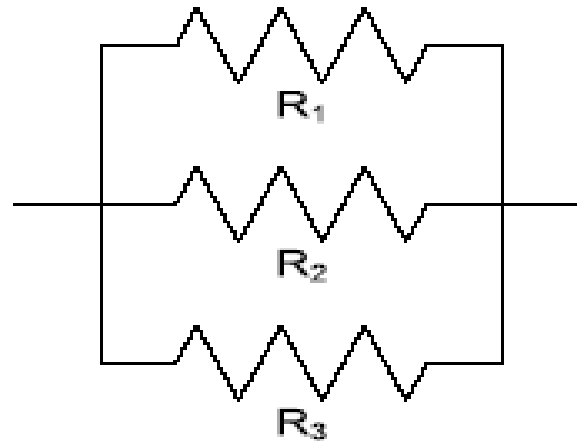


$P_{re}$  – the same voltage on the smaller resistor  $R_{re}$ .

# Applications of Resistors

- Filters
- Switch circuitry
- Integrators
- Amplifiers
- ...
- Voltage divider
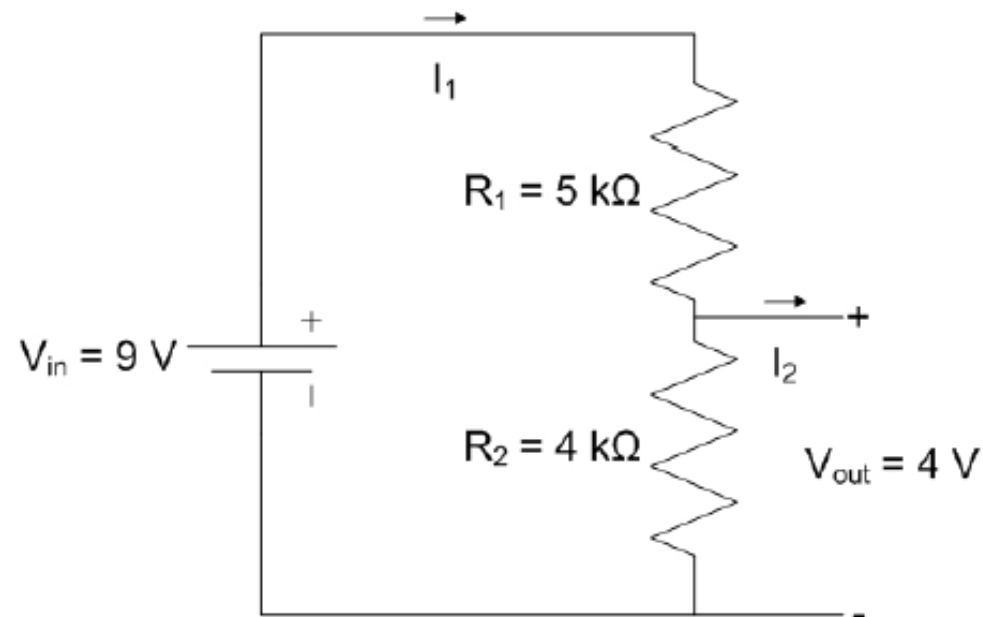
# Voltage Divider


A voltage divider is designed to create an output voltage which is proportional to the input voltage.



Example of a voltage divider
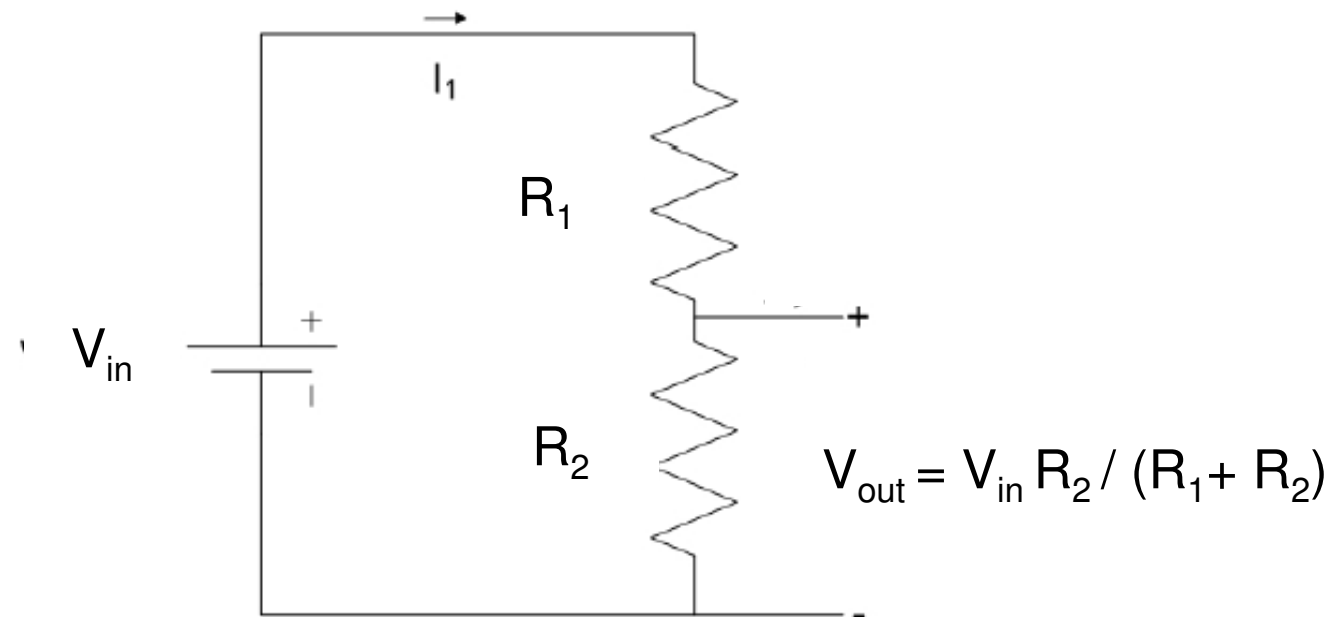
# Voltage Divider


A voltage divider is designed to create an output voltage which is proportional to the input voltage.



Example of a voltage divider



# Potentiometers

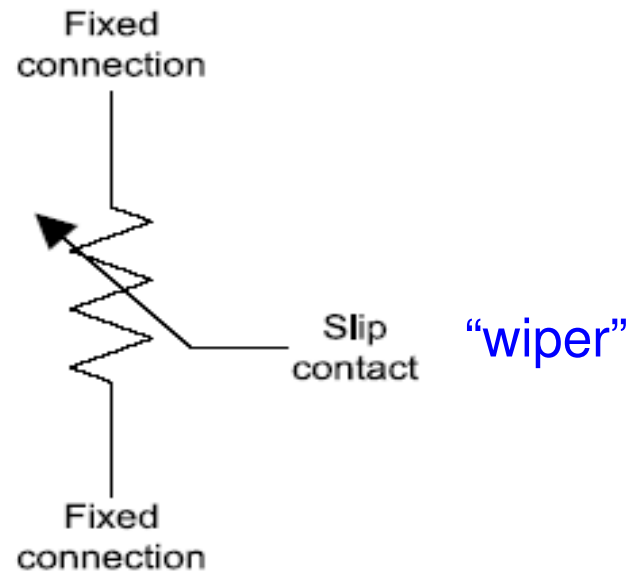


Schematic symbol of a potmeter


- Adjustable resistors - Potmeters
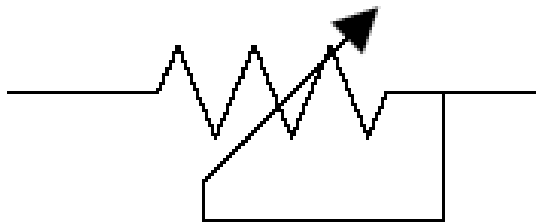
# Applications of Potmeters

- An adjustable resistance value for filtering (next chapter)
- Adjustable voltage divider (e.g. in an audio amplifier)



“Plain” adjustable resistance value

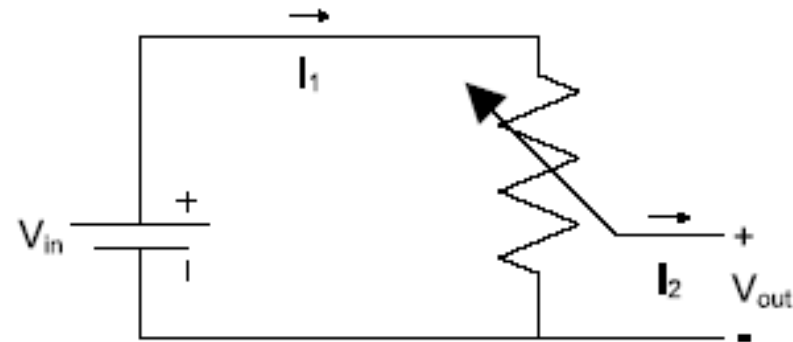

adjustable voltage divider

# Types of Potmeters

- Turn potmeters - with a portable rotation axis



from [wikipedia.org](https://en.wikipedia.org)


- Slide potmeters




from [www.made-in-china.com](http://www.made-in-china.com)

- Linear - the resistance value is proportional to the degree of rotation or slide
- Logarithmic - regulate volume in an audio amplifier
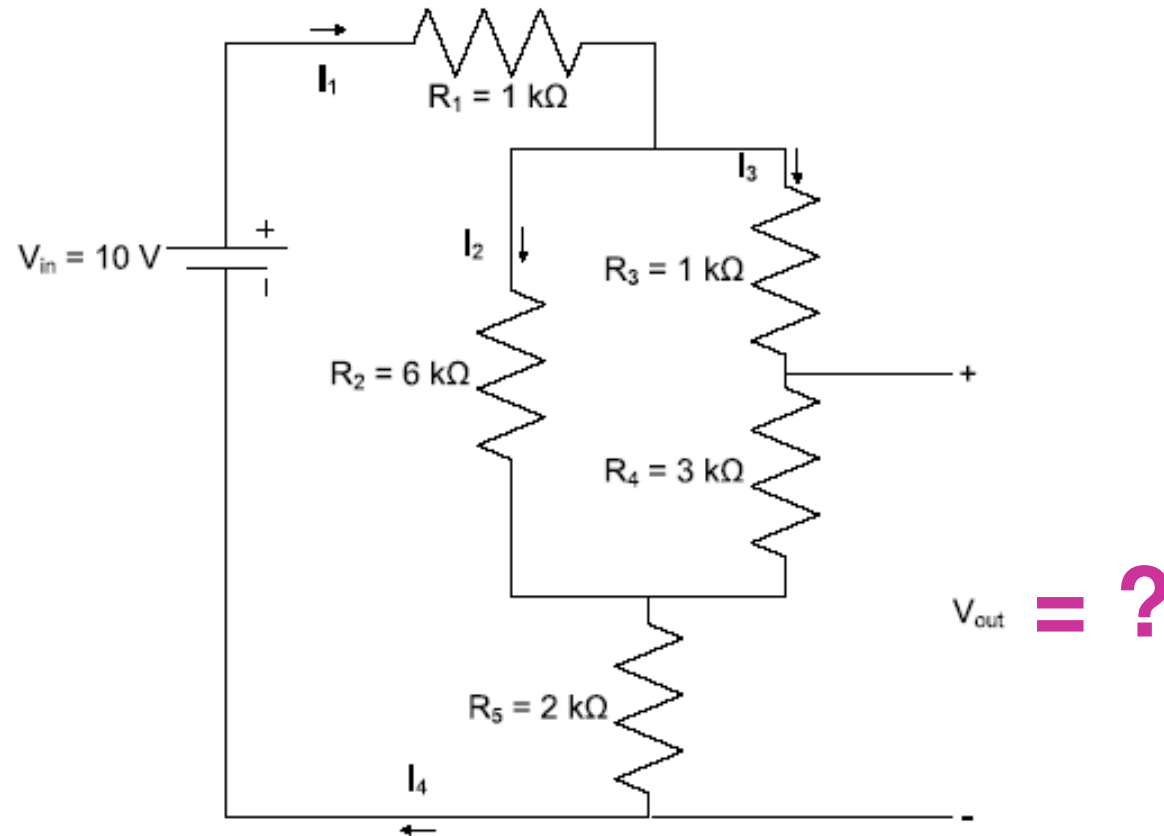
# Calculation of Replacement Resistance Value



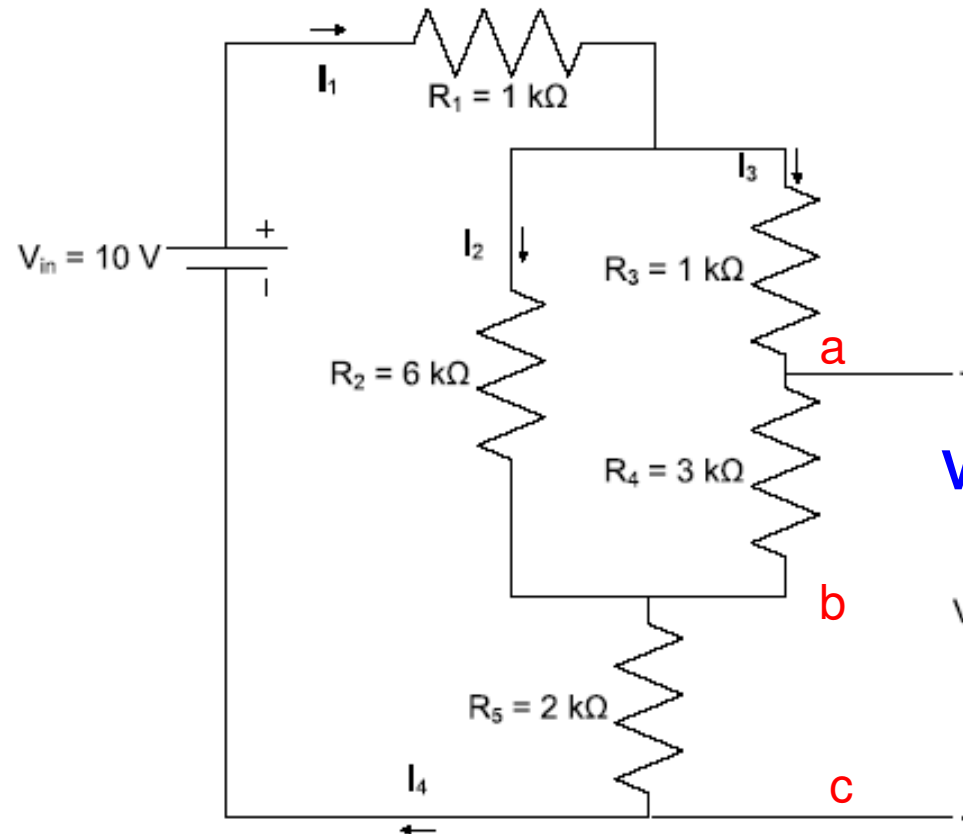
# Calculation of Replacement Resistance Value



$$V_{out} = V_{ac} = V_{ab} + V_{bc}$$

$$V_{out} = V_{R4} + V_{R5}$$
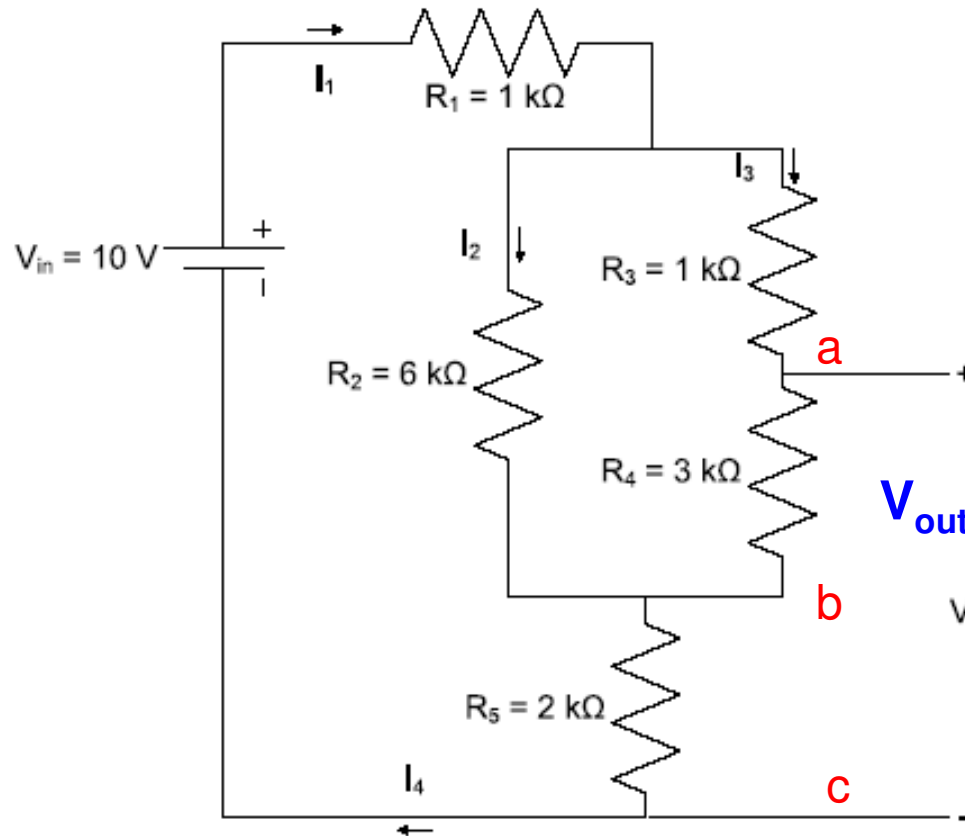
# Calculation of Replacement Resistance Value



Ohm's law

$$V_{out} = I_1 \cdot R_5 + I_3 \cdot R_4$$

$$I_1 = I_4 = I_2 + I_3$$


$$V_{out} = V_{ac} = V_{ab} + V_{bc}$$

$$V_{out} = V_{R4} + V_{R5}$$

$$I_1 = ?$$

$$I_3 = ?$$

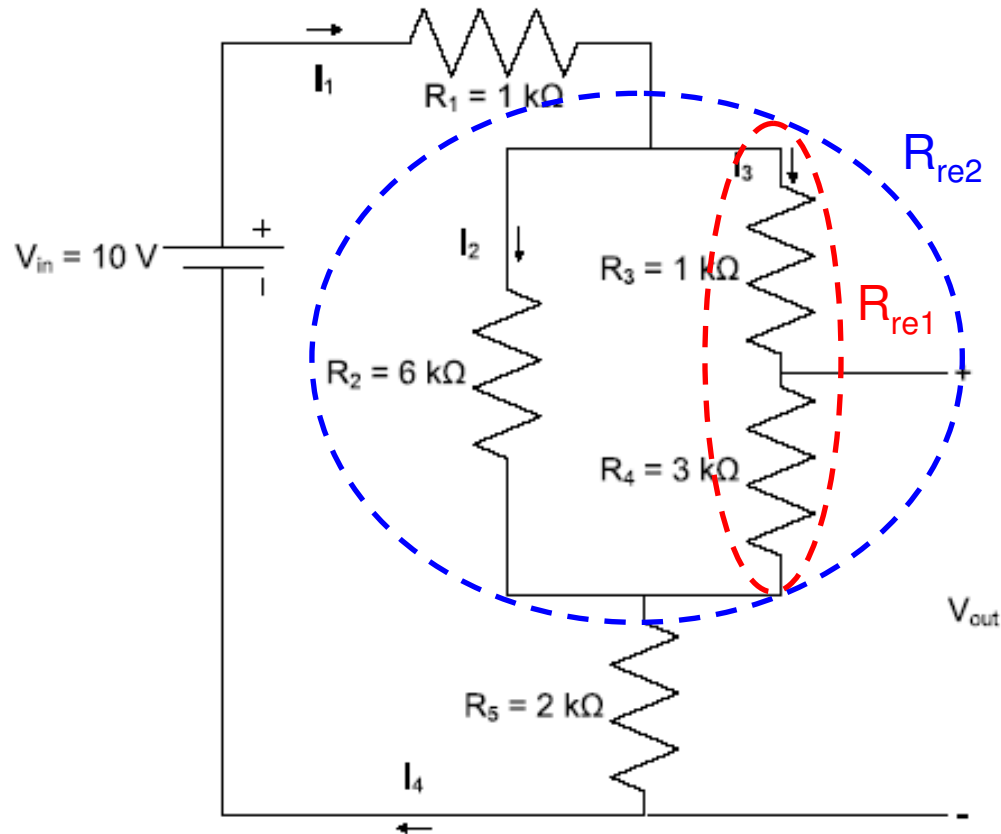
# Calculation of Replacement Resistance Value



$$R_{re1} = R_3 + R_4 = 4\text{ k}\Omega$$

$$R_{re2} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_{r1}}} = 2.4\text{ k}\Omega$$
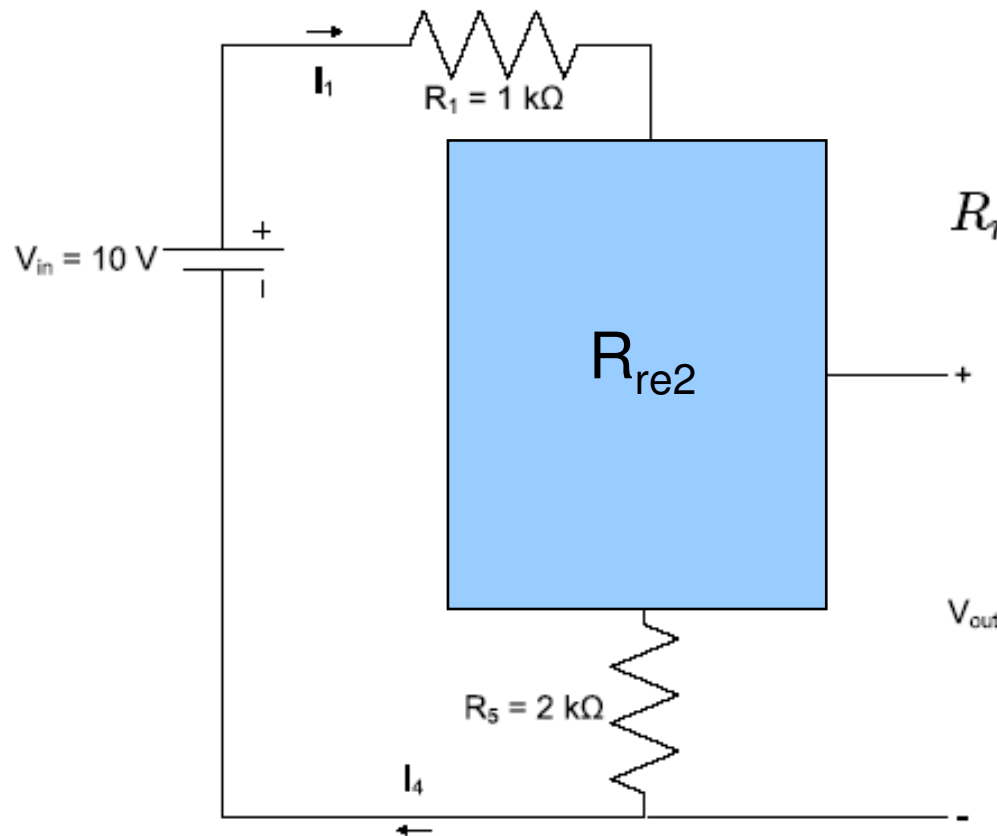
# Calculation of Replacement Resistance Value




$$R_{retotal} = R_1 + R_{r2} + R_5 = 5.4\text{ k}\Omega$$

$$I_1 = \frac{V_{in}}{R_{retotal}} = 1.85\text{ mA}$$


**Next,  $I_3$  ?**


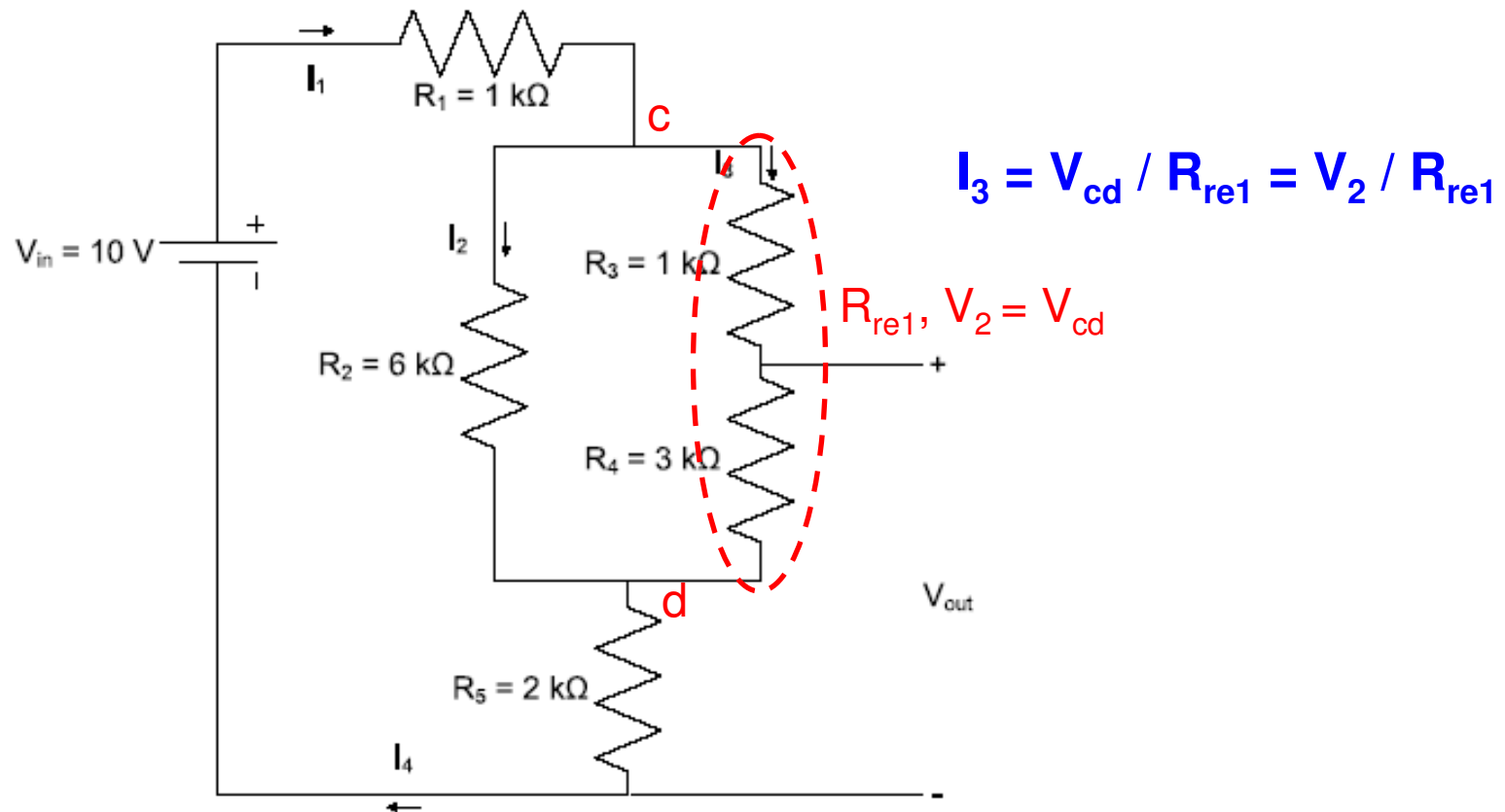
# Calculation of Replacement Resistance Value



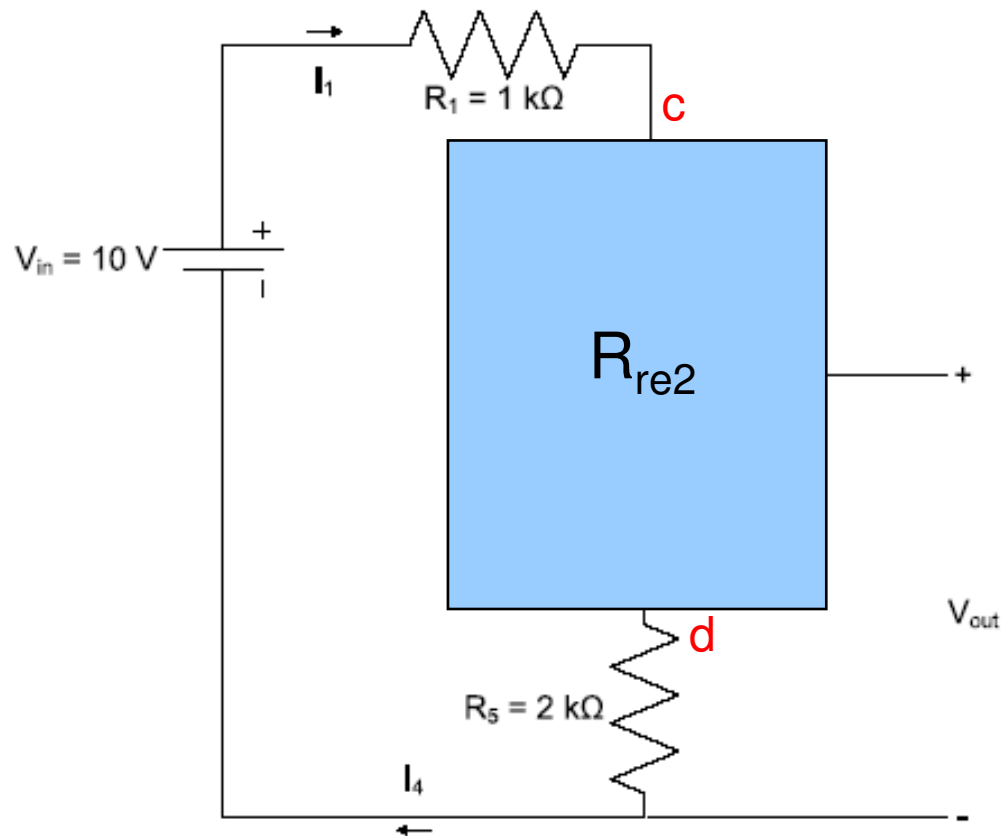
# Calculation of Replacement Resistance Value




$$V_2 = V_{cd} = I_1 \cdot R_{re2}$$

$$V_2 = 1.85\text{ mA} \cdot 2.4\text{ k}\Omega = 4.44\text{ V}$$
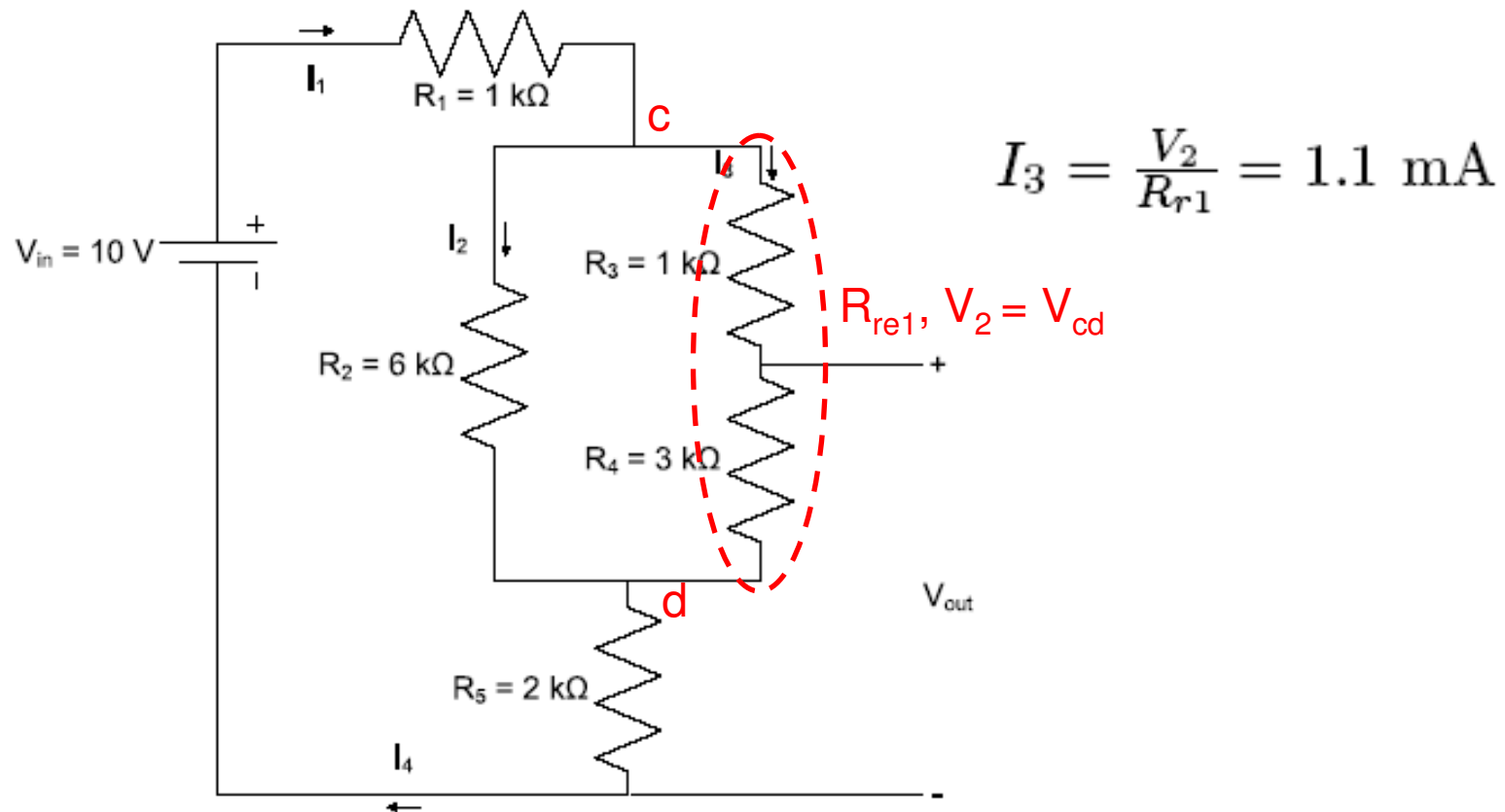
# Calculation of Replacement Resistance Value


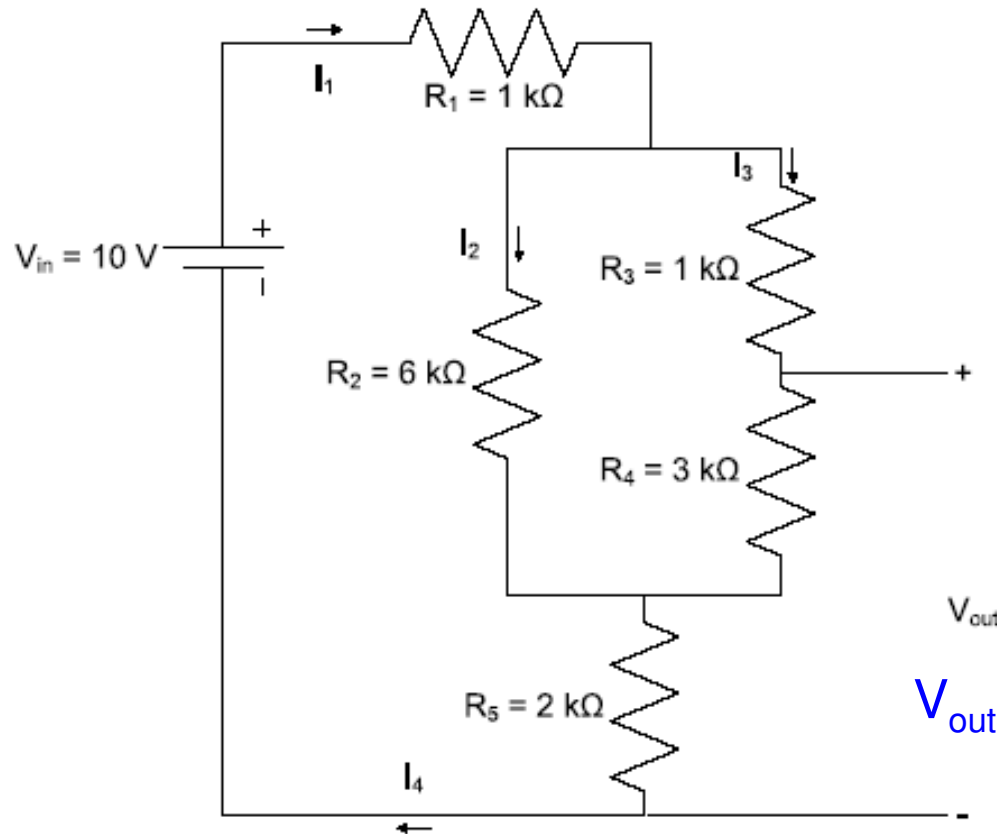
# Calculation of Replacement Resistance Value



Ohm's law

$$V_{out} = I_1 \cdot R_5 + I_3 \cdot R_4$$

$$I_1 = \frac{V_{in}}{R_{total}} = 1.85\text{ mA}$$

$$I_3 = \frac{V_2}{R_{r1}} = 1.1\text{ mA}$$

$$V_{out} = 1.85\text{ mA} \cdot 2\text{ k}\Omega + 1.1\text{ mA} \cdot 3\text{ k}\Omega = 7.04\text{ V}$$