

Cross Section Creative Technology

Operational Amplifiers
Sensors and Actuators

What are Amplifiers?



From www.gadgetuniverse.com

What are Amplifiers?

- An **amplifier** is any device that use a small amount of energy to generate a larger amount of energy.
(e.g. amplification of a signal that your mobile phone received on its antenna, ECG measurement, ect.)
- **Gain** is a measure of amplification.
 $G = V_{out} / V_{in}$ In specs, $G = 10 \cdot \log_{10} (P_{out}/P_{in})$, with a unit of dB.

Types of amplifiers:

- Electronic amplifiers
 - Transistor amplifiers
 - Operational amplifiers
 - ...
- Optical amplifiers
- ...

What are Operational Amplifiers?

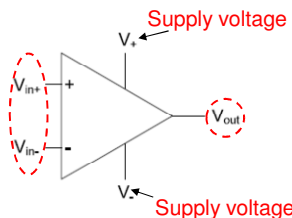


Figure 10.1: Schematic symbol for an operational amplifier.

$$V_{out} = G \cdot (V_{in+} - V_{in-}) \quad (10.1)$$

- G is the gain.
- When no other components are connected, G is in the order of 10^5 to 10^7 ! (**open-loop** voltage gain)
- The output voltage is limited by the +/- supply voltages.
(clipping)

Closed-loop Model of Opamp

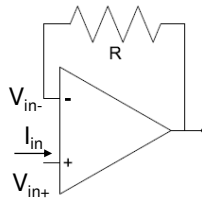


Figure 10.2: Operational amplifier with in a negative feedback configuration using a resistor.

- $I_{in} = 0$ (high input impedance)
- $V_{in+} = V_{in-}$

Closed-loop Model of Opamp

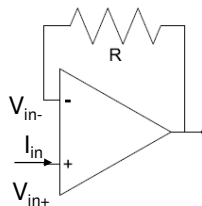


Figure 10.2: Operational amplifier with in a negative feedback configuration using a resistor.

- $V_{in+} > V_{in-}$: the output voltage increase V_{in-}
- $V_{in+} < V_{in-}$: the output voltage decrease V_{in-}
- $I_{in} = 0$
- $V_{in+} = V_{in-}$

Op amps and Inverting Amplifiers

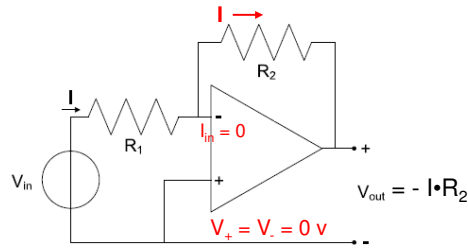


Figure 10.3: Operational amplifier used in an inverting amplifier circuit.

$$I = V_{in} / R_1$$

$$V_{out} = -\frac{R_2}{R_1} V_{in} \quad (10.2)$$

Op amps and Inverting Amplifiers

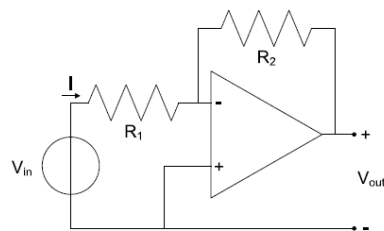



Figure 10.3: Operational amplifier used in an inverting amplifier circuit.

$$V_{out} = -\frac{R_2}{R_1} V_{in} \quad (10.2)$$

$$G = -R_2 / R_1$$

- $R_2 > R_1$, Inverting amplifier
- $R_2 < R_1$, Inverting attenuator
- $R_2 = R_1$, Inverter

Op amps and Summing Amplifiers

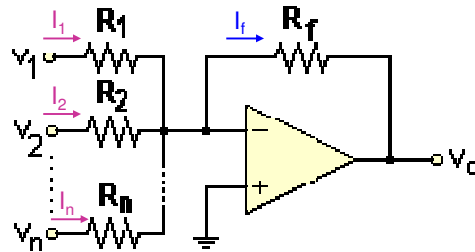

$$V_o = - (V_1/R_1 + V_2/R_2 + \dots + V_n/R_n) \cdot R_f$$

Op amps and Non-inverting Amplifiers

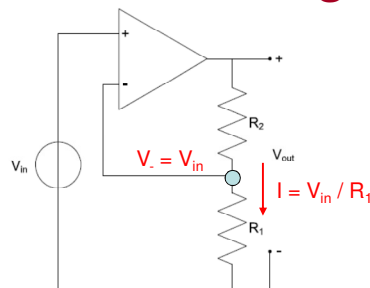


Figure 10.4: Operational amplifier used in a non-inverting amplifier circuit.

$$V_{out} = I (R_1 + R_2)$$

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in} \quad (10.3)$$

Op amps and Non-inverting Amplifiers

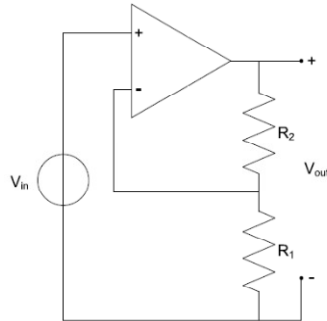


Figure 10.4: Operational amplifier used in a non-inverting amplifier circuit.

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in} \quad (10.3)$$

$$G = 1 + R_2 / R_1$$

Operational Amplifiers

Datasheet will provide you with the parameters needed to make a good choice of which opamp to use.

Amplifying AC Signal

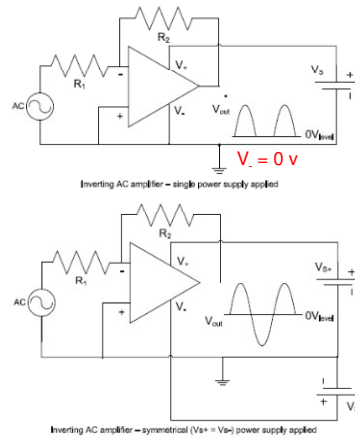


Figure 10.5: Operational amplifier used as AC amplifier.

Op amps and Comparators

- Circuits performing comparison are called comparators.
- Clipping amplifiers (open-loop) can be used for comparators.

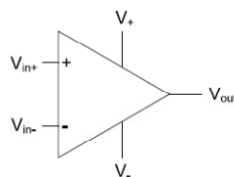


Figure 10.1: Schematic symbol for an operational amplifier.

$$\begin{aligned} V_{in+} > V_{in-}, & V_{out} = V_{+} \\ V_{in+} < V_{in-}, & V_{out} = V_{-} \end{aligned}$$

Op amps and Comparators

- Circuits performing comparison are called comparators.
- Clipping amplifiers (open-loop) can be used for comparators.


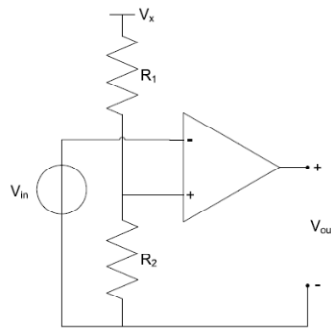


Figure 10.6: Operational amplifier used in a comparator circuit with static comparison.

Op amps and Comparators
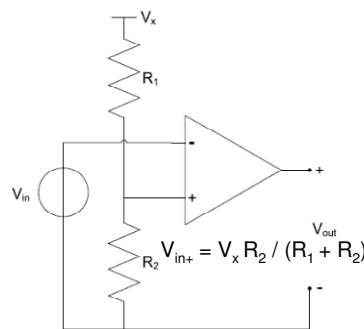
$$V_{out} = G \cdot (V_{in+} - V_{in-}) \quad (10.1)$$



$$V_{in} < \frac{R_2}{R_1 + R_2} V_x \quad V_{out} = V_{s+}$$

$$V_{in} > \frac{R_2}{R_1 + R_2} V_x \quad V_{out} = V_{s-}$$


How to obtain the following?

$$V_{in} > \frac{R_2}{R_1 + R_2} V_x \quad V_{out} = V_{s+}$$

$$V_{in} < \frac{R_2}{R_1 + R_2} V_x \quad V_{out} = V_{s-}$$

Figure 10.6: Operational amplifier used in a comparator circuit with static comparison.

Op amps and Comparators

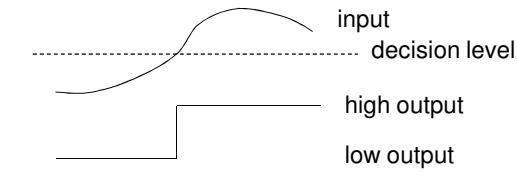

Output of a comparator when the input is clean.


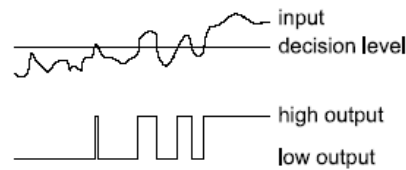


Figure 10.7: The output of a comparator toggles when the input is noisy.

Op amps and Comparators

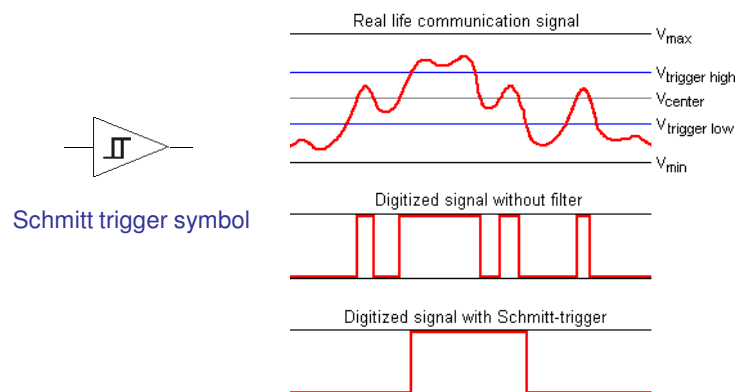A Schmitt trigger is a comparator circuit that incorporates positive feedback.





Schmitt trigger symbol

From www.lammertbies.nl/comm/info/Schmitt-trigger.html
http://en.wikipedia.org/wiki/Schmitt_trigger

Op amps and Comparators

$$V_{\text{out, high}} = 10 \text{ V}$$

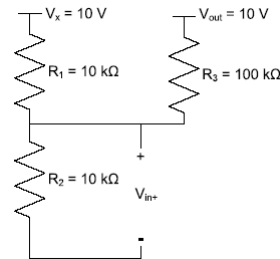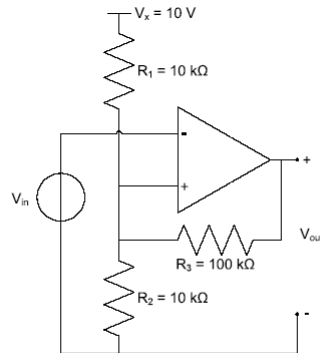



$$V_{\text{in}+} = \frac{R_2}{R_2 + \frac{R_1 \cdot R_3}{R_1 + R_3}} \cdot V_x = 5.24 \text{ V}$$

Output changes from high to low, when $V_{\text{in}} > V_{\text{in}+}$ (5.24 V).

Figure 10.9: An opamp with feedforward in a static comparator circuit.

Op amps and Comparators

$$V_{\text{out, low}} = 0 \text{ V}$$

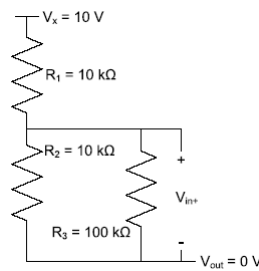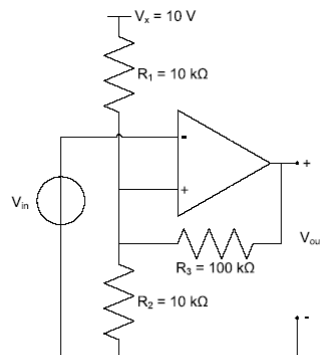

$$V_{\text{in}+} = \frac{\frac{R_2 \cdot R_3}{R_2 + R_3}}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}} \cdot V_x = 4.76 \text{ V}$$

Output changes from low to high, when $V_{\text{in}} < V_{\text{in}+}$ (4.76 V).

Figure 10.9: An opamp with feedforward in a static comparator circuit.

Op amps and Comparators


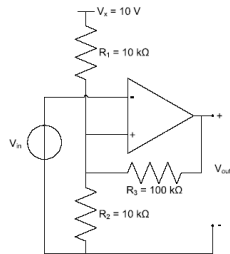



Figure 10.9: An opamp with feedforward in a static comparator circuit.

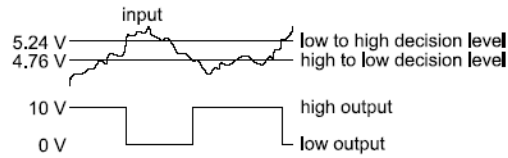

The output of a comparator with feedforward does not make the output toggle for noisy input signals.

Sensors and Actuators

Human Senses

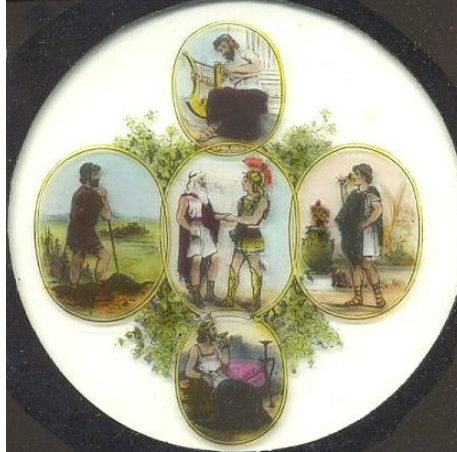

from http://www.phoenixmasonry.org/masonicmuseum/glossary/images/slide_77_the_five_senses.jpg

What are Sensors and Actuators?

- Electronic sensors and actuators are components that enable interaction between the physical world and electrical circuits.
- A **sensor** converts a physical phenomenon into an electrical signal for processing.
- An **actuator** converts a processed electrical signal to a physical phenomenon.

Why Sensors and Actuators?

- Design intelligent products
- Extend the sensing beyond our human senses
 - Standard frequency range of human hearing: 20 Hz - 20 kHz
 - Limited temperature range a human being can feel
 - etc.
- Benefit our life
 - Health
 - Security
 - Entertainment
 - etc.

Sensing the Environment

- Sensors have been used to explore the changes in the environment.
- Provide direct information on physical parameters:
 - Lightness
 - Pressure
 - Temperature
 - Magnetic field
 - etc.
- Give indirect indication on emotion of human:
 - comfortable
 - excited
 - angry
 - etc.

Actuators

- An **actuator** converts a processed electrical signal to a physical phenomenon.
- Actuators can have both continuous and discrete values. - switch light on / off or use a dimmer
- Actuators are all around us:
 - speakers
 - electric motors
 - heating elements
 - light sources
 - etc.

A Central Heating System

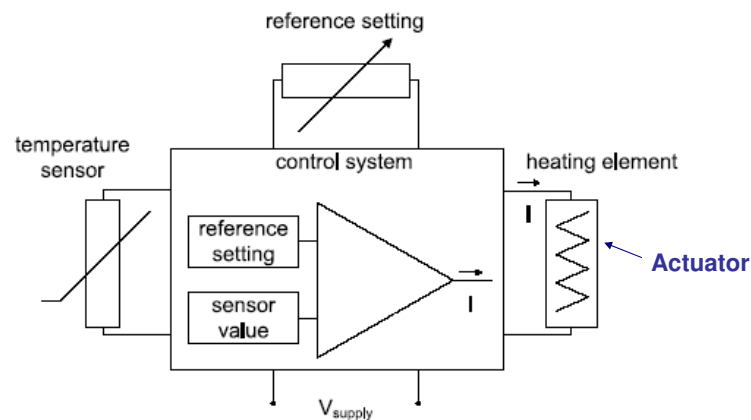


Figure 11.1: Closed-loop temperature control system.

Example Design Project

Light Dependent Sensors



Green street, B1.1 project, designed by Ivo Wouters, Bart van Oorschot, Jasper Blom, Maarten Woudstra, Rick Paffen and Rik Hermans

<http://www.youtube.com/watch?v=rOWoT-PJPil>

TU/e technische
universiteit
eindhoven

Wei Chen

Light Dependent Resistor (LDR)

The resistance of a LDR depends on the lightness:

- When the lightness increases, the value of the resistance decreases.
- Typical resistance values: 5.5 k Ω in dark, 55 Ω in a light environment

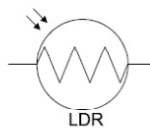


Figure 11.3: Schematic symbol for an LDR


TU/e technische
universiteit
eindhoven

Wei Chen

Light Dependent Resistor (LDR)

The resistance of a LDR depends on the lightness:

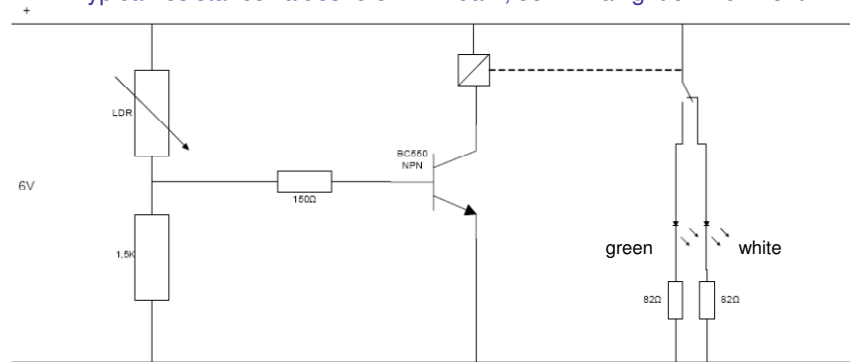- When the lightness increases, the value of the resistance decreases.
- Typical resistance values: 5.5 k Ω in dark, 55 Ω in a light environment



LDR for light color switching control - Student project "Green Street"
 designed by Ivo Wouters, Bart van Oorschot, Jasper Blom, Maarten Woudstra, Rick Paffen and Rik Hermans

<http://www.youtube.com/watch?v=rOWoT-PJPiI>

TU/e technische universiteit eindhoven

Wei Chen

Temperature - sensitive: NTC and PTC

- NTC: Resistance value decreases when temperature increases.
- PTC: Resistance value increases when temperature increases.




Figure 11.8: Schematic symbol for NTCs and PTCs.

TU/e technische universiteit eindhoven

Wei Chen

Temperature - sensitive: NTC and PTC

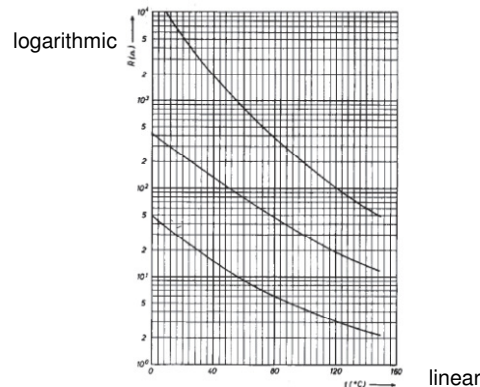
- **NTC**: Resistance value decreases when temperature increases.
- **PTC**: Resistance value increases when temperature increases.



Resistance vs. temperature for three different NTCs.

Example Design Project

Pressure Sensors

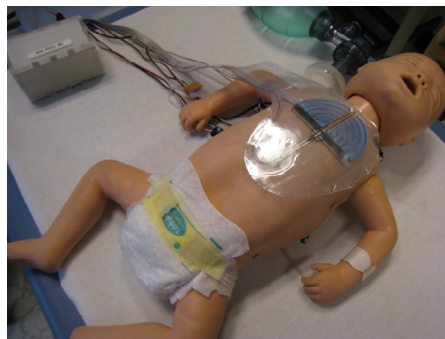

Rhythm of life (I&II), M1.1 and B2.1 project, designed by Floris Kimman, Maarten Geraets, Yening Jin, Nicolas Nelson, Mark Thielen, Yi Xue
<http://www.idemployee.id.tue.nl/w.chen/papers/wchen-TITB-Journal10.pdf>

Smart Textile

- Health monitoring



Textile sensor in a belt to monitor child's ECG and respiration.
- Ghent University, Belgium

- Protection for special tasks, e.g. Jackets for fire fighter



from: bensguide.gpo.gov/images/ben/ben_fireman.jpg

- Emotion reflection (e.g. body motion monitoring, color changing T-shirt)

TU/e technische universiteit eindhoven

Wei Chen

Example Design Project

Smart Textile Sensors



Smart jacket for NICU, M2.2 project, designed by Sibrecht Bouwstra
<http://www.smartjacket.id.tue.nl/>

TU/e technische universiteit eindhoven

Wei Chen

E-atelier

- <http://www.eatelier.nl/>
- <http://www.eatelier.nl/components>
- <http://www.eatelier.nl/example-circuits/blog>